



北京大学
PEKING UNIVERSITY

22530007

人工智能与芯片设计

2-Verilog HDL与数字集成电路基础

燕博南
2023秋


Computer Engineering Basics

- Why AI chip?
- Logic Gates? What is computer hardware?
- Flip-Flops? Registers?
- How computer executes program?
- What is GPU?
- Difference between CPU, FPGA, GPU
- <http://www.asic-world.com/verilog/veritut.html>

Part 1

Verilog HDL grammar, operators, synthesizable design

Digital Circuit Design Flow

 

Basic Building - Module

```
1  // single-line comments
2  /* multi-line
3  comments
4  */
5  module name(
6      input a,b,
7      input [31:0] c,
8      output z,
9      output reg [3:0] s
10 ); ← Don't forget ";" here
11 // declarations of internal signals, registers
12 // combinational logic: assign
13 // sequential logic: always @ (posedge clock)
14 // module instances
15 endmodule
```

In Verilog we design modules, one of which will be identified as our top-level module. Modules usually have named, directional ports (specified as `input`, `output`) which are used to communicate with the module.


- Format: HDL ignores space “ ”, it only recognize “;”

Wires & Registers

Wires


```
1 // 2-to-1 multiplexer with dual-polarity outputs
2 module mux2(
3     input a,b,sel,
4     output z,zbar
5 );
6 // again order doesn't matter (concurrent execution!)
7 // syntax is "assign LHS = RHS" where LHS is a wire/bus
8 // and RHS is an expression
9 assign z = sel ? b : a;
10 assign zbar = ~z;
11 endmodule
```

Directly connect!

 

Regs
 
```
1 // 2-to-1 multiplexer with dual-polarity outputs
2 module weird_mux2(
3     input a,b,sel,
4     output z,
5     output reg zbar
6 );
7 // again order doesn't matter (concurrent execution!)
8 // syntax is "assign LHS = RHS" where LHS is a wire/bus
9 // and RHS is an expression
10 assign z = sel ? b : a;
11
12 always @(posedge clk) begin
13     zbar = ~z;
14 end
15
16 endmodule
```



Secrets of Wires & Regs

- Without “reg” declaration, variables are always wires
- Reg can only be output and inside signals
- Assignment:
 - Wires can only be changed using “assign” outside “always”
 - Regs can only be changed inside “always”

```
10  assign zbar = ~z;
```

```
12  always @(posedge clk) begin
13      zbar = ~z;
14  end
```

Operators

Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
	+	Unary plus
	-	Unary minus
Logical	!	Logical negation
	&&	Logical and
Relational		Logical or
	>	Greater than
	<	Less than
	>=	Greater than or equal
	<=	Less than or equal
Equality	==	Equality
	!=	inequality
Shift	>>	Right shift
	<<	Left shift
	<<<, >>>	Arithmetic shift

Reduction	~	Bitwise negation
	~&	nand
		or
	~	nor
	^	xor
	^~	xnor
	~^	xnor

Concatenation	{ }	Concatenation
Conditional	?	conditional

What are the difference between (logic) shift and arithmetic shift?

Numeric Constants

Constant values can be specified with a specific width and radix:

123 // default: decimal radix, 32-bit width

'd123 // 'd = decimal radix

1'd3 ??

'h7B // 'h = hex radix

'o173 // 'o = octal radix

is 1'd1

'b111_1011 // 'b = binary radix, “_” are ignored

'hxx // can include X, Z or ? in non-decimal constants

16'd5 // 16-bit constant 'b0000_0000_0000_0101

11'h1X? // 11-bit constant 'b001_XXXX_ZZZZ

By default constants are unsigned and will be extended with 0's on left if need be (if high-order bit is X or Z, the extended bits will be X or Z too).

You can specify a signed constant as follows:



8'shFF // 8-bit twos-complement representation of -1

To be absolutely clear in your intent it's usually best to explicitly specify the width and radix.

Hierarchy: module instances

```
1 // 4-to-1 multiplexer
2 module mux4(input d0,d1,d2,d3, input [1:0] sel, output z);
3   wire z1,z2;
4   // instances must have unique names within current module.
5   // connections are made using .portname(expression) syntax.
6   // once again order doesn't matter...
7   mux2 m1(.sel(sel[0]),.a(d0),.b(d1),.z(z1)); // not using zbar
8   mux2 m2(.sel(sel[0]),.a(d2),.b(d3),.z(z2));
9   mux2 m3(.sel(sel[1]),.a(z1),.b(z2),.z(z));
10  // could also write "mux2 m3(z1,z2,sel[1],z,)" NOT A GOOD IDEA!
11 endmodule
```


- Write all original names (style requirement)
- Connection are concurrently executed

  

Example 1: A counter

```
1 module counter (  
2   out      , // Output of the counter  
3   enable   , // enable for counter  
4   clk      , // clock Input  
5   reset    , // reset Input  
6 );  
7  
8 output [1:0] out; //Output Ports  
9 input enable, clk, reset; //Input Ports  
10  
11 reg [1:0] out; //Internal Variables  
12  
13 always @(posedge clk)  
14 if (reset) begin  
15 |   out <= 2'b0 ;  
16 end else if (enable) begin  
17 |   out <= out + 1;  
18 end  
19  
20 endmodule
```

What is the timing diagram?

 

- Beware of “before” & “after” clock edge

Verification: Simulation & Testbench


Design:

```
1 module counter (  
2   out      , // Output of the counter  
3   enable   , // enable for counter  
4   clk      , // clock Input  
5   reset    // reset Input  
6 );  
7  
8 output [1:0] out; //Output Ports  
9 input enable, clk, reset; //Input Ports  
10  
11 reg [1:0] out; //Internal Variables  
12  
13 always @(posedge clk)  
14 if (reset) begin  
15   out <= 2'b0 ;  
16 end else if (enable) begin  
17   out <= out + 1;  
18 end  
19  
20 endmodule
```


Testbench:

```
1 `timescale 1ns/1ps  
2 module Testbench;  
3  
4   wire [1:0] OUT;  
5   reg EN, CLK, RST;  
6  
7   initial CLK = 0;  
8   always #2 CLK=~CLK;  
9  
10  initial begin  
11    #1  
12    EN = 0;  
13    RST = 1;  
14    #4  
15    EN = 1;  
16    RST = 0;  
17    #(4*7)  
18    EN = 0;  
19  end  
20  
21  counter u1(  
22    .out (OUT)      , // Output of the counter  
23    .enable (EN)    , // enable for counter  
24    .clk  (CLK)     , // clock Input  
25    .reset (RST)    // reset Input  
26  );  
27  
28 endmodule
```

Testbench has no ports



Blocking and Non-blocking

 

```
1 // shift register
2 reg q1,q2,out;
3 always @(posedge clk) begin
4     q1 = in;
5     q2 = q1;
6     out = q2;
7 end
```

Wrong!

```
1 // shift register
2 reg q1,q2,out;
3 always @(posedge clk) q1 <= in;
4 always @(posedge clk) q2 <= q1;
5 always @(posedge clk) out <= q2;
```



Correct!

Part 2


Finite State Machine

Finite State Machine


- Hardware/Circuits

 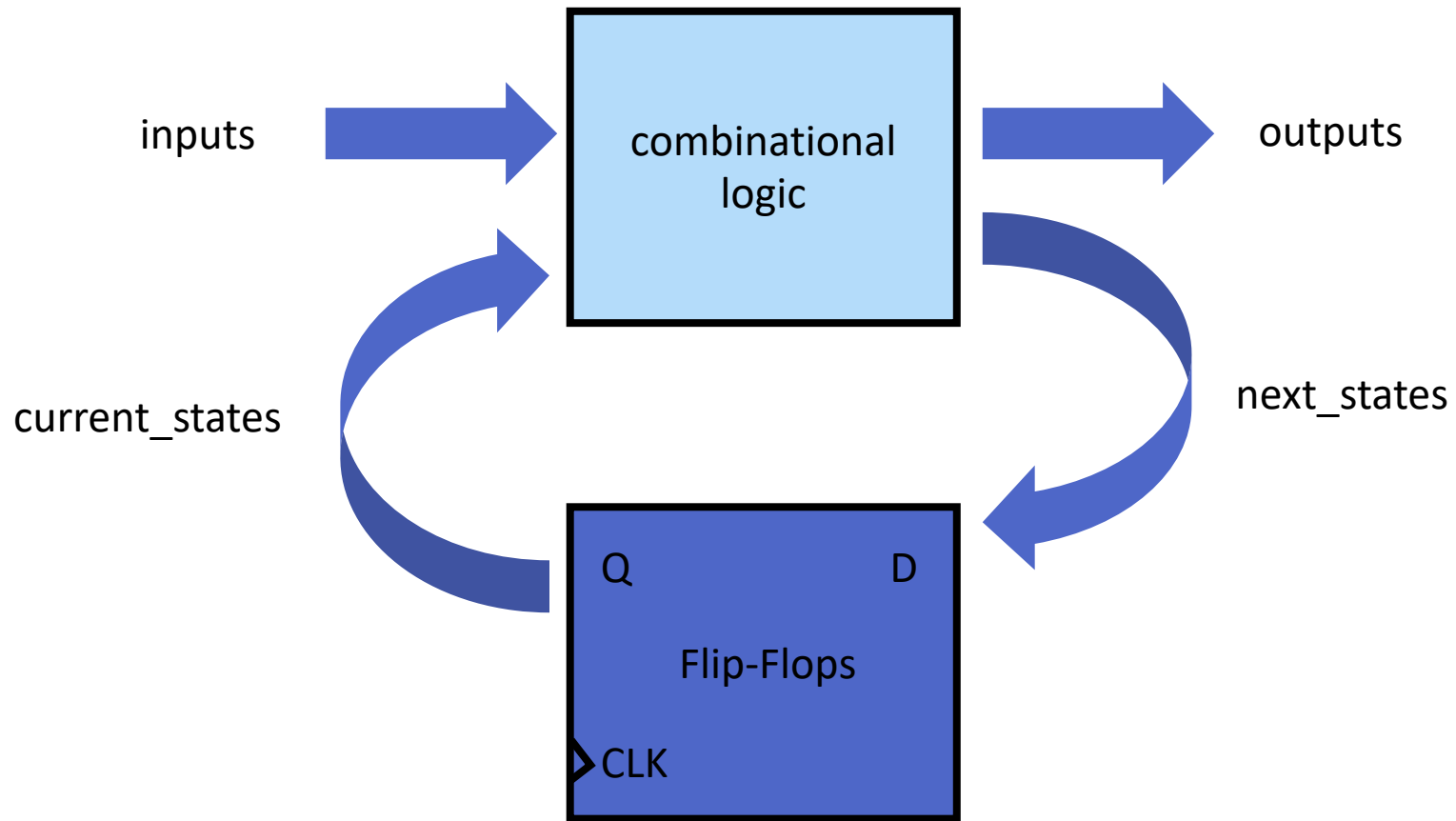

Design Methodologies & Templates

 

Step 1: define states

 


Step 2: draw state-transfer diagram

```
1 module safe_state_machine (
2     input  clk, data_in, reset,
3     output reg [1:0] data_out
4 );
5
6 reg [1:0] state;
7 // Declare states
8 parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3;
9 // Output depends only on the state
10 always @ (state) begin
11     case (state)
12         S0: data_out = 2'b01;
13         S1: data_out = 2'b10;
14         S2: data_out = 2'b11;
15         S3: data_out = 2'b00;
16         default:
17             data_out = 2'b00;
18     endcase
19 end
20
21
22
23
24
25 // Determine the next state
26 always @ (posedge clk or posedge reset) begin
27     if (reset)
28         state <= S0;
29     else
30         case (state)
31             S0: state <= S1;
32             S1: if (data_in)
33                 state <= S2;
34                 else
35                     state <= S1;
36             S2: if (data_in)
37                 state <= S3;
38                 else
39                     state <= S1;
40             S3: if (data_in)
41                 state <= S2;
42                 else
43                     state <= S3;
44         endcase
45     end
46 end
```

Step 3: fill in the template

FSM Example 1 Passcode Detector

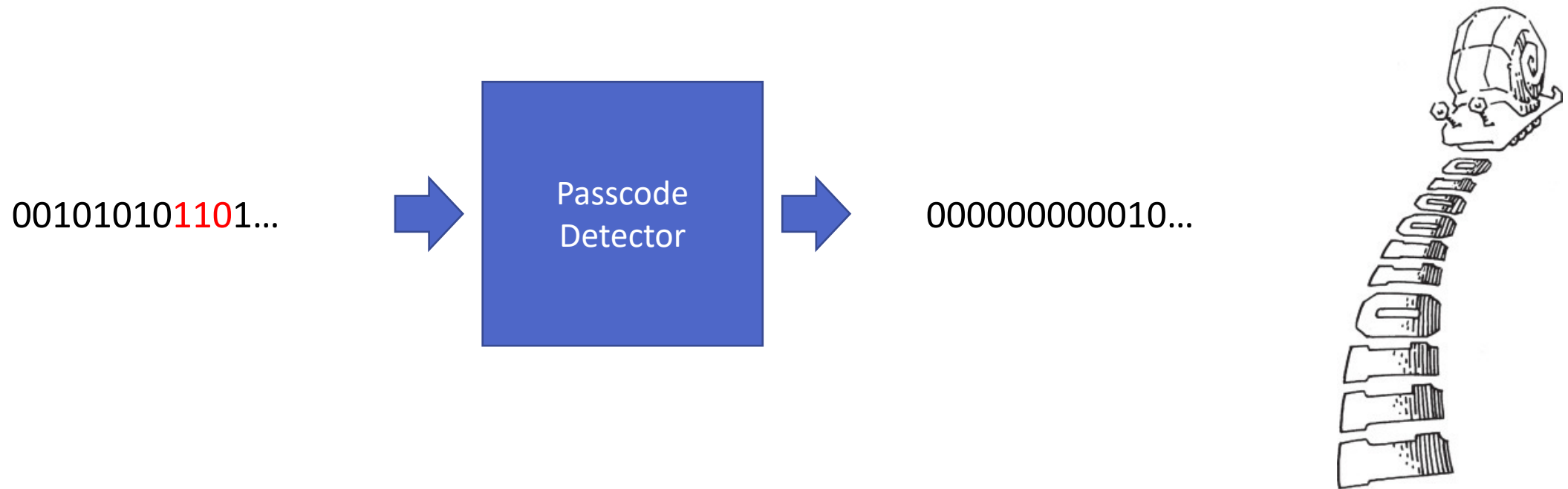
Question: build circuits that outputs 1 pulse, whenever receives “110”



FSM Example 1 – Step 1 & 2

Question: build circuits that outputs 1 pulse, whenever receives “110”

Input: (input, rst^b)

 

FSM Example 1 – Step 3


Question: build circuits that outputs 1 pulse, whenever receives “110”

```
1  module PasscodeDetector (  
2      input  clk, data_in, rstb,  
3      output reg data_out  
4  );  
5  
6      reg [1:0] state;  
7      // Declare states  
8      parameter STAT_IDLE = 0,  
9              STAT_R1 = 1,  
10             STAT_R2 = 2,  
11             STAT_R3 = 3;  
12      // Output depends only on the state  
13      always @ (state) begin  
14          if(state == STAT_R3) begin  
15              data_out <= 1; // alarming!  
16          end  
17          else begin  
18              data_out <= 0;  
19          end  
20      end
```


```
22      // Determine the next state  
23      always @ (posedge clk) begin  
24          if (~rstb)  
25              state <= STAT_IDLE;  
26          else  
27              case (state)  
28                  STAT_IDLE: begin  
29                      if(data_in==1) begin  
30                          state <= STAT_R1;  
31                      end  
32                  end  
33                  STAT_R1: begin  
34                      if (data_in==1)  
35                          state <= STAT_R2;  
36                      else  
37                          state <= STAT_IDLE;  
38                  end  
39                  STAT_R2: begin  
40                      if (data_in==0)  
41                          state <= STAT_R3;  
42                      else  
43                          state <= STAT_R2;  
44                  end  
45                  STAT_R3: begin  
46                      if(data_in==1) begin  
47                          state <= STAT_R1;  
48                      end  
49                      else begin  
50                          state <= STAT_IDLE;  
51                      end  
52                  end  
53              endcase  
54          end  
55      endmodule
```

FSM Example 2 Auto Chip Testing Environment

 Push button to test Function 1, Function 2, Function 3, ... in series



FSM Example 2 Step 1&2

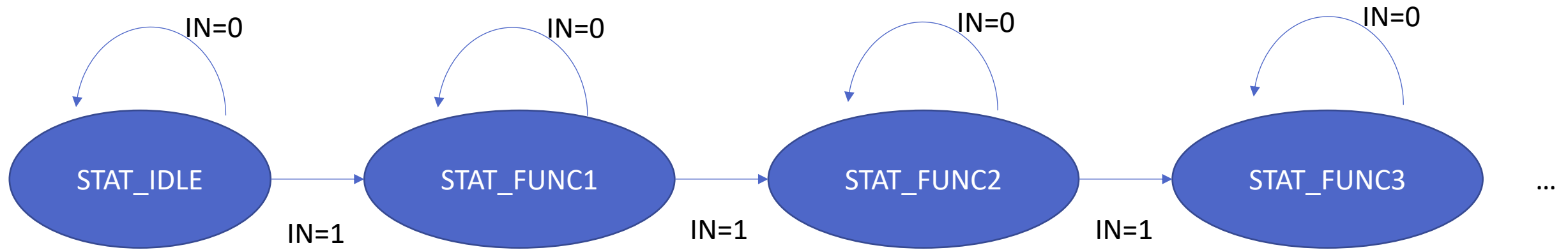

Step 3 is so easy... that you can fill it yourself.

Another Question

Philosophy behind:

Use “state variable” to label timing

Another Q:

How to generate custom waveform
after entering some state?

Solution: setup an counter variable

Do everything at its pace

[! DO NOT ABUSE. This may cause
large comparing logic.]



Possibility of Nested State Machine!

```
1  always @ (posedge clk or posedge reset) begin
2      if (reset)
3          state <= S0;
4      else begin
5          case (state)
6              S0:
7                  data_out = 2'b01;
8              S1: begin
9                  if(cnt==10'd1) begin
10                     //do what you want
11                 end
12                 else if (cnt<=10'd5) begin
13                     //do what you want
14                 end
15                 else if (cnt<=10'd20) begin
16                     //do what you want
17                 end
18                 else begin
19                     //do what you want
20                 end
21             end
22         end
23         S2:
24             data_out = 2'b11;
25         S3:
26             data_out = 2'b00;
27         default:
28             data_out = 2'b00;
29     endcase
30 end
31 end
```

A practical application – Vending Machine

All selections are ¥ 0.30

The machine make changes

Inputs:

- ¥ 0.25
- ¥ 0.10
- ¥ 0.05

Outputs

- Dispense can
- Dispense ¥ 0.10
- Dispense ¥ 0.05



Example from MIT

A practical application – Vending Machine

- A starting (idle) state:



- A state for each possible amount of money captured:



- What's the maximum amount of money captured before purchase?


25 cents (just shy of a purchase) + one quarter (largest coin)



- States to dispense change (one per coin dispensed):



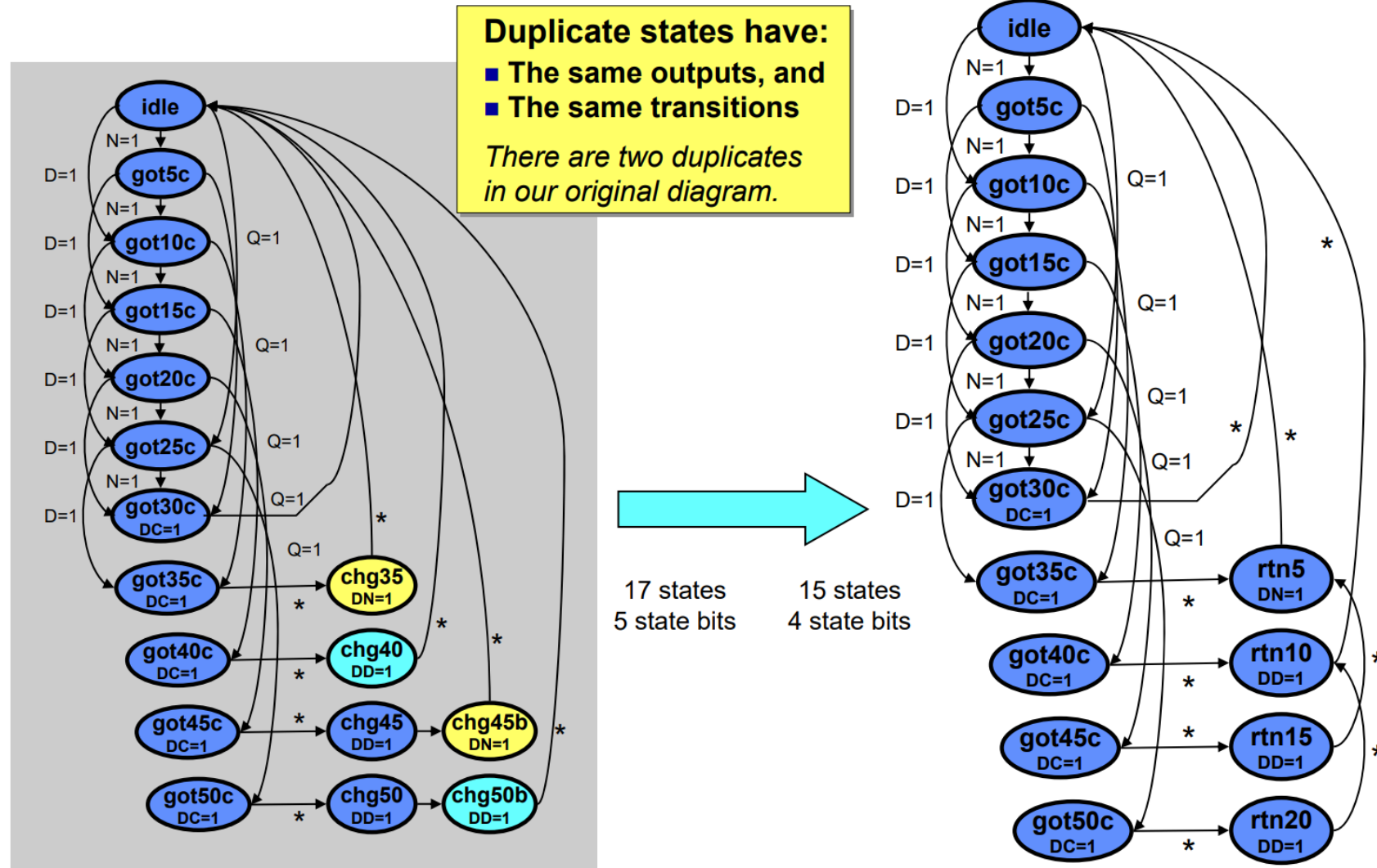A practical application – Vending Machine



Discussion

- State Machine vs. AI
 - State machines exhaustively cover all cases, which is impossible in AI agent design.
- State machine is appropriate for small scale designs.
- Nested state machines:
 - normally, do not nest inside FSM in >2 folds.
 - Otherwise, too complicated **timing path** dependency.